

SDR – Part 7

MCU and DDS Schematic













Here is the schematic of the MCU and the DDS.













Instead of using a lot of wires to connect everything I used net labels.

Page 1 and 2 of this document are set up to print as A4.

Page 3 is setup to print and A3.

Samuel

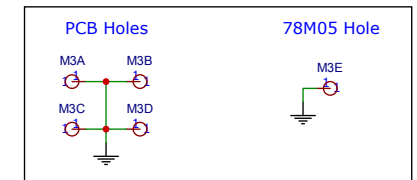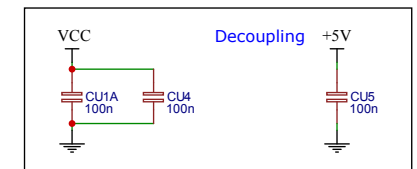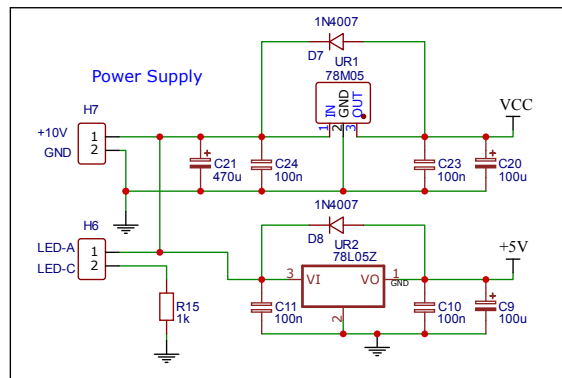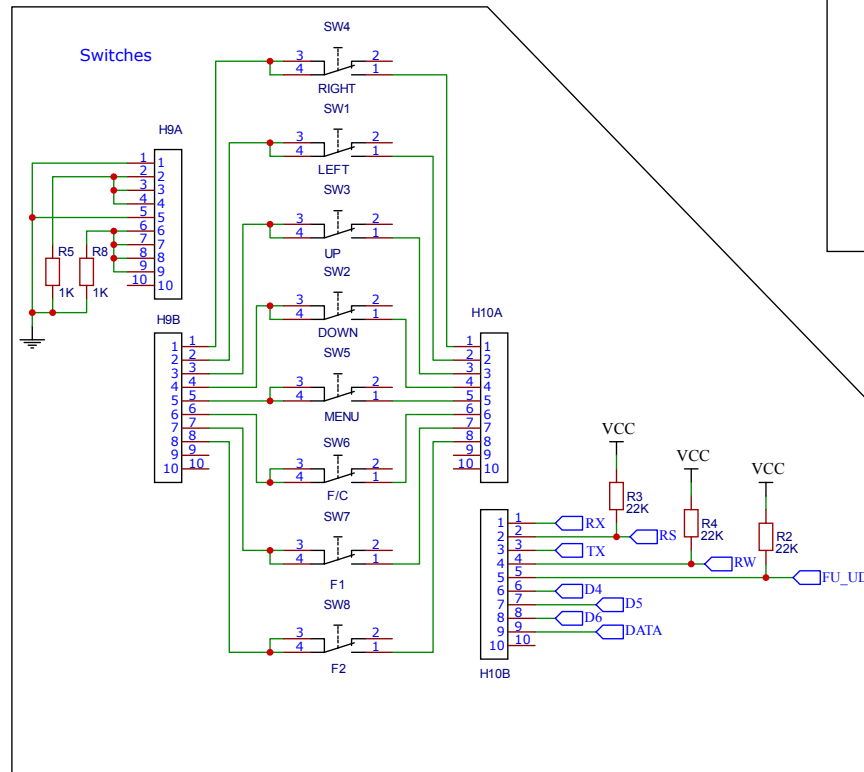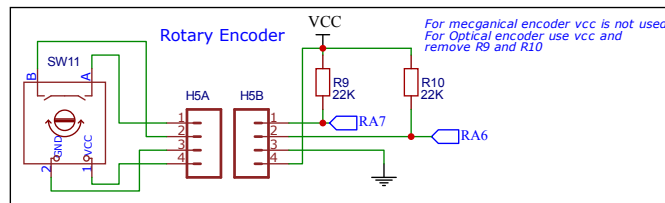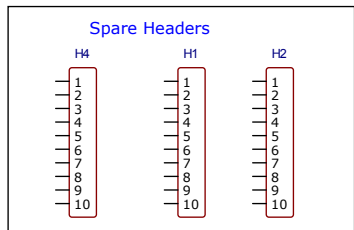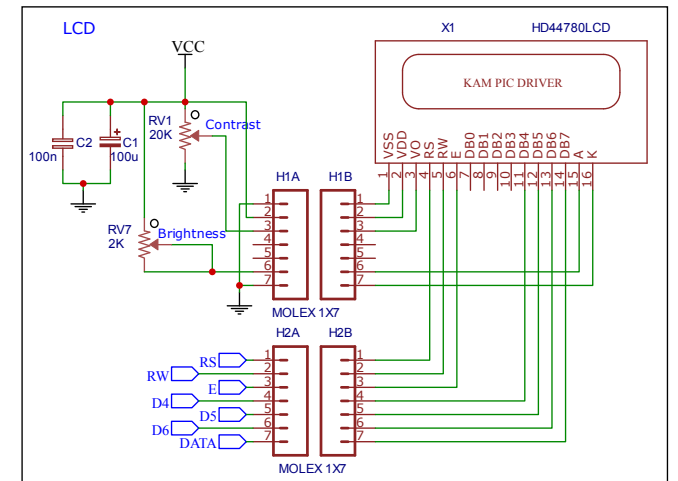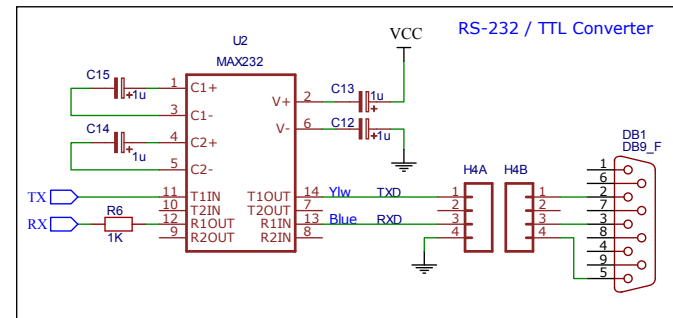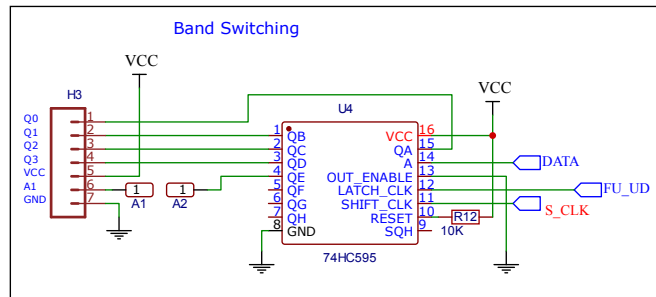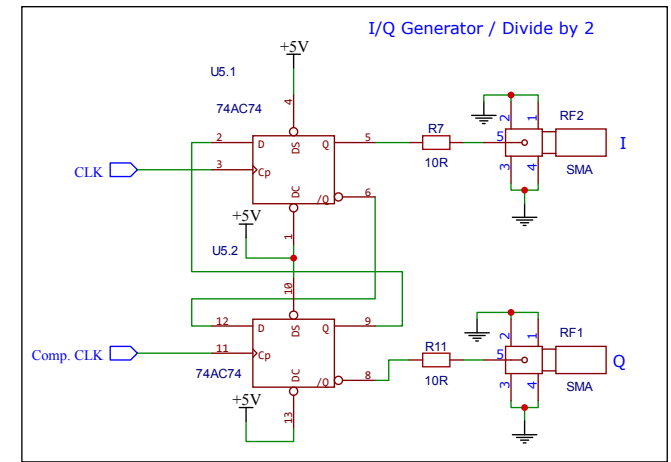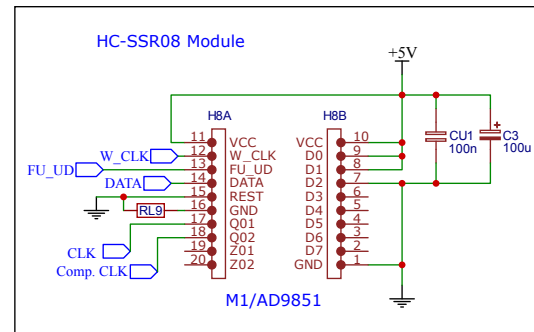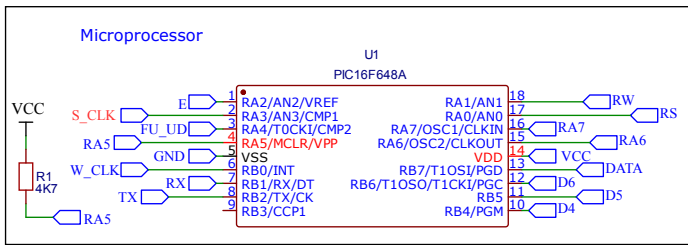

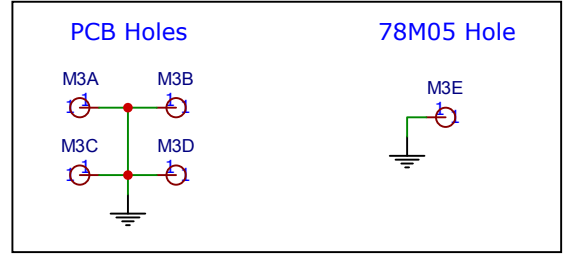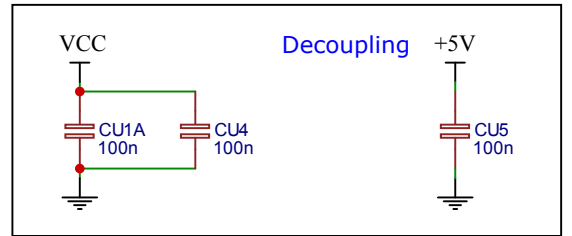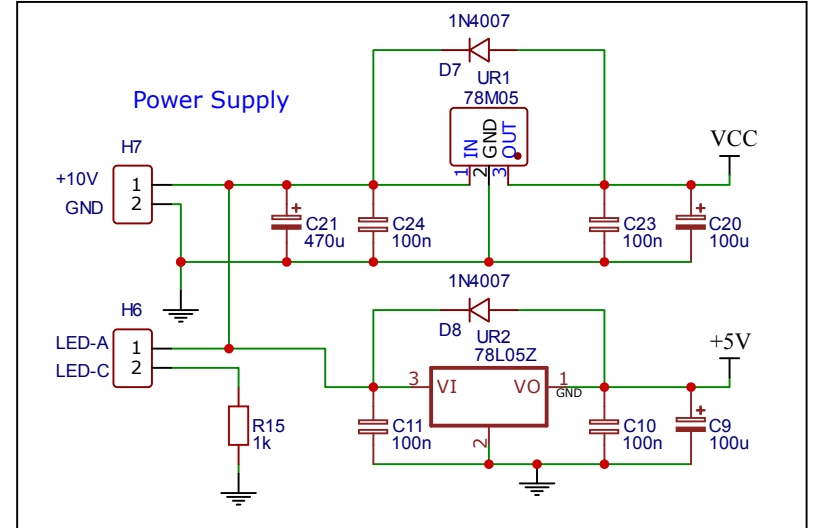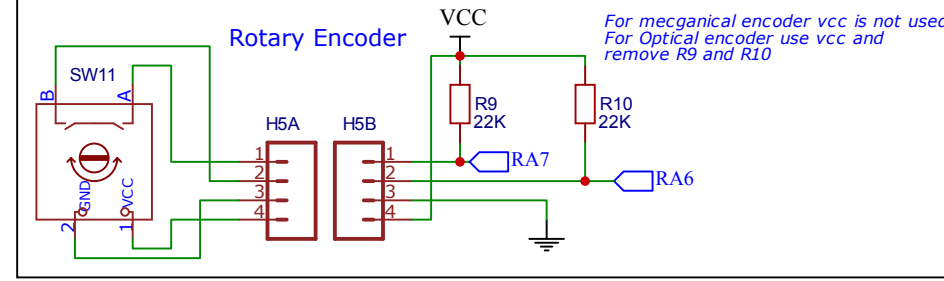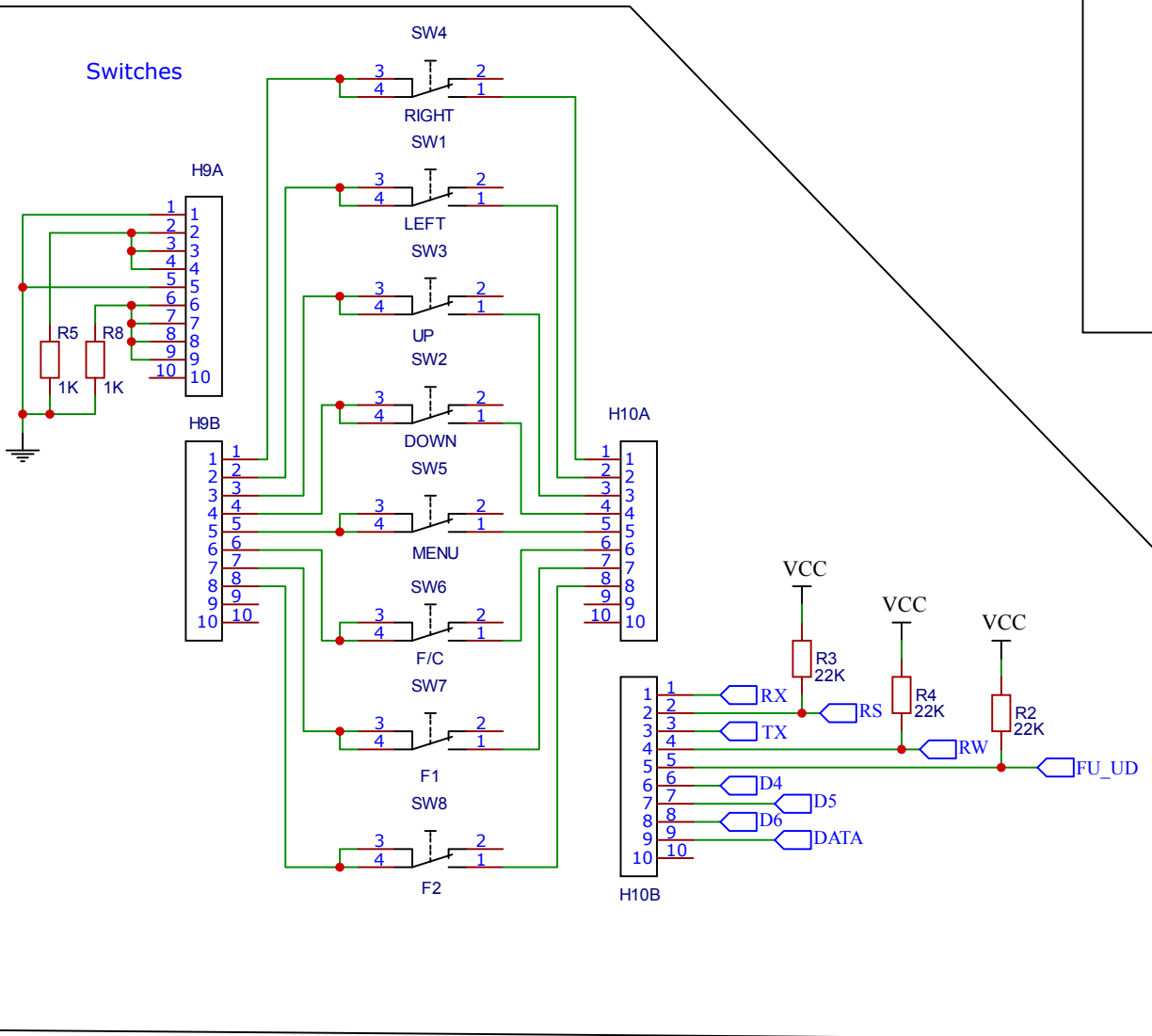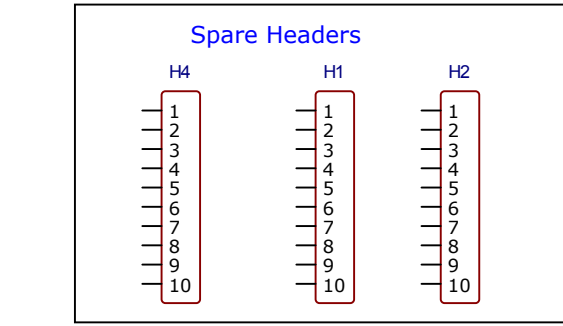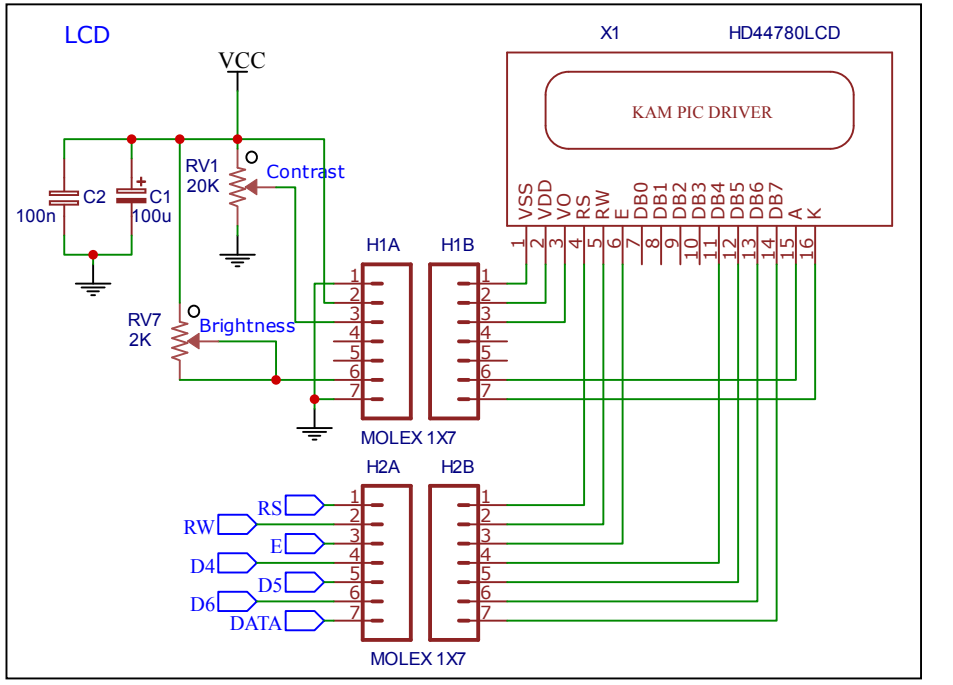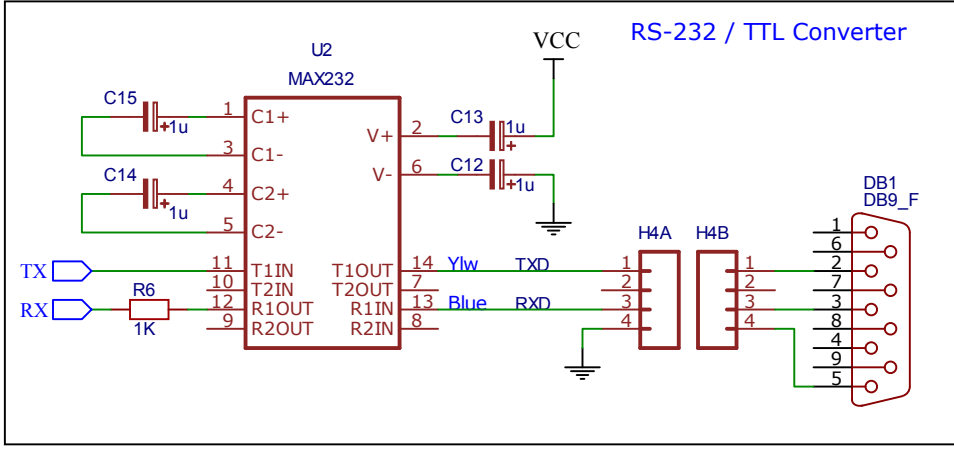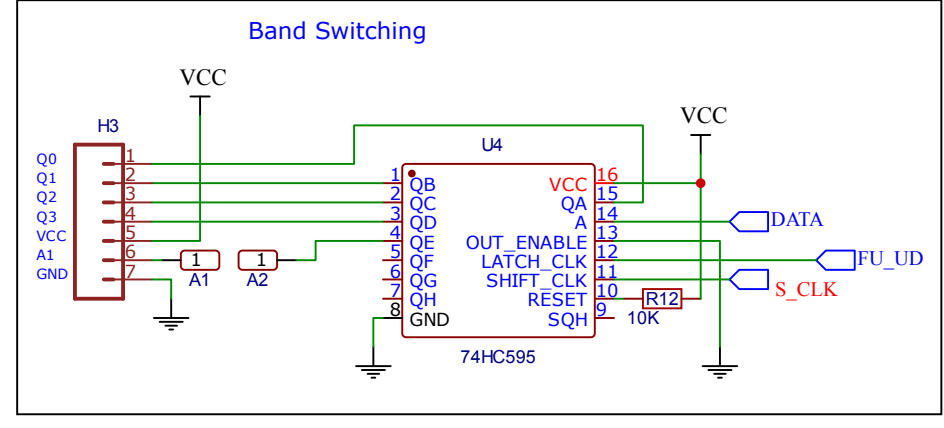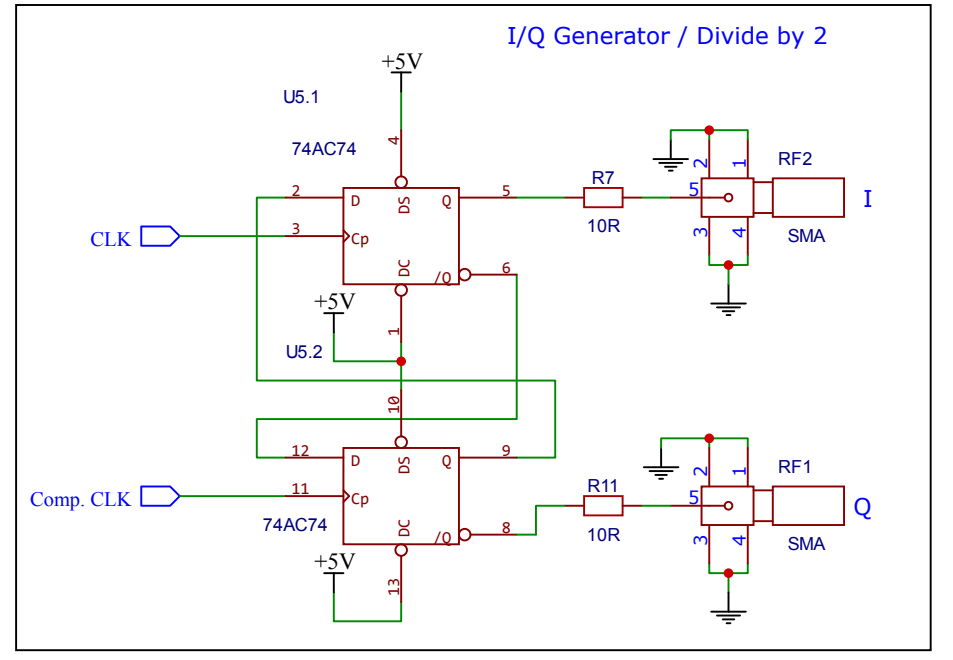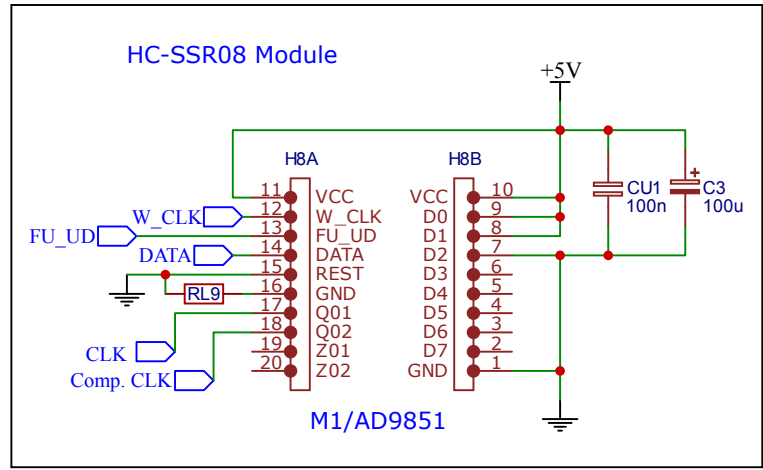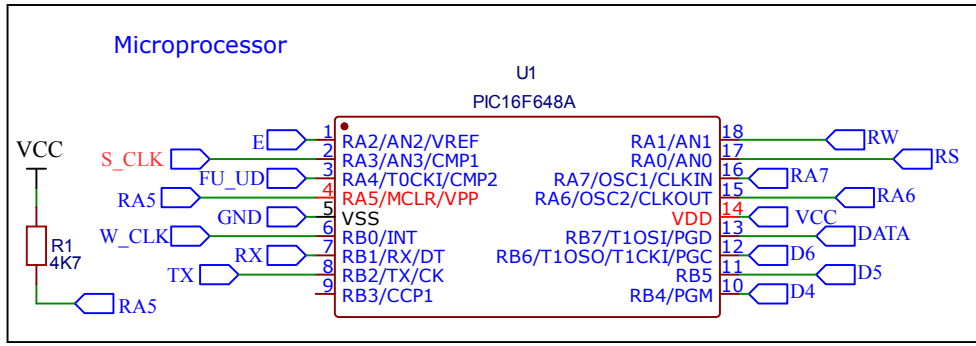

TITLE:	CPU and DDS	REV:	1.0
Company:	Dr. R	Sheet:	1/1
Date:	2021-07-04	Drawn By:	samuel.ritchie.8

